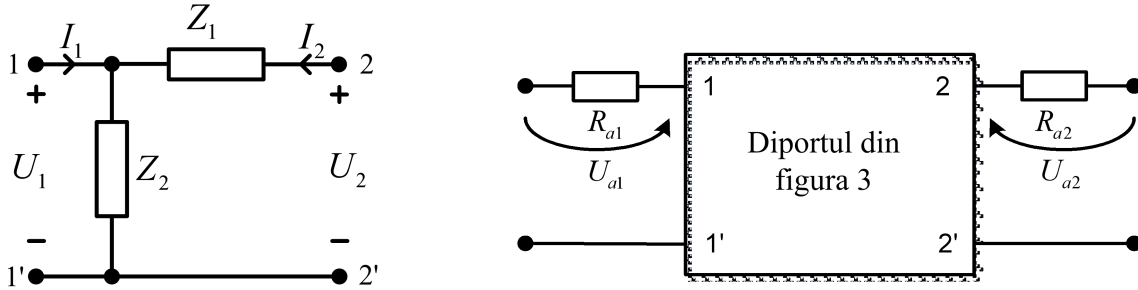



Sample Subjects for SS2 Laboratory Colloquium

1. Determine the parameters A for the two-port network shown in the figure. For the indirect measurement of the currents at port 1 and port 2, measure the resistance values R_{a1} at port 1 and R_{a2} at port 2 using a multimeter set to ohmmeter mode. The measurements are performed with alternating current at a frequency of 10 kHz, and the voltage applied from the generator is 5 Vrms. For the circuit implementation, the following resistances are used: $R_{a1} = 10\Omega$, $R_{a2} = 10\Omega$, $Z_1 = 150\Omega$, $Z_2 = 600\Omega$.




Measured values									Calculated values based on measurements				
The condition $I_2 = 0$				The condition $U_2 = 0$					A_{11}	A_{12}	A_{21}	A_{22}	ΔA
U_1	U_2	U_{a1}	I_1	U_1	U_{a1}	I_1	U_{a2}	I_2					
[V]	[V]	[V]	[mA]	[V]	[V]	[mA]	[V]	[mA]	-	[k Ω]	[mS]	-	-

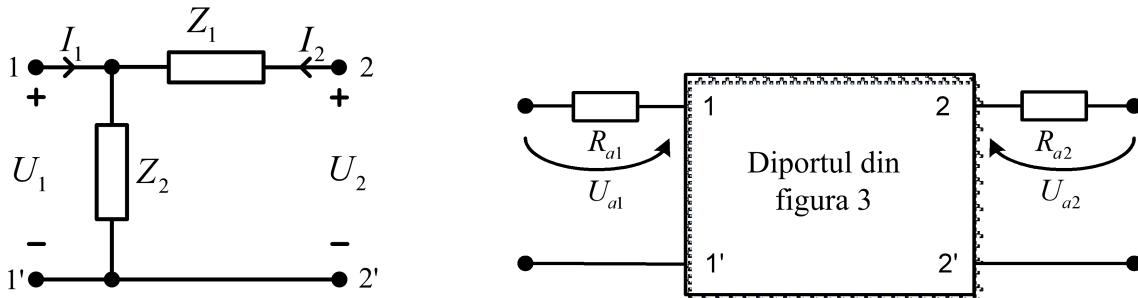2. Determine the parameters Z for the two-port network shown in the figure. For the indirect measurement of the currents at port 1 and port 2, measure the resistance values R_{a1} at port 1 and R_{a2} at port 2 using a multimeter set to ohmmeter mode. The measurements are performed with alternating current at a frequency of 10 kHz, and the voltage applied from the generator is 5 Vrms. For the circuit implementation, the following resistances are used: $R_{a1} = 10\Omega$, $R_{a2} = 10\Omega$, $Z_1 = 150\Omega$, $Z_2 = 600\Omega$.



Valori măsurate						Calculated values based on measurements				
The condition $I_2 = 0$			The condition $I_1 = 0$			Z_{11}	Z_{12}	Z_{21}	Z_{22}	$\frac{ Z_{12} - Z_{21} }{Z_{12}}$
U_1	U_2	I_1	U_1	U_2	I_2					
[V]	[V]	[mA]	[V]	[V]	[mA]	[k Ω]	[k Ω]	[k Ω]	[k Ω]	-

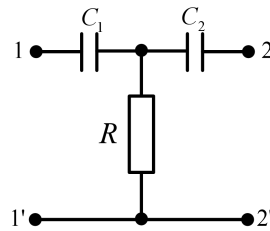3. Determine the parameters Y for the two-port network shown in the figure. Work is done with alternating current at a frequency of 10 kHz, and the voltage applied from the generator is 5 Vrms. The following resistors and capacitors are used for the circuit implementation: $R = 600\Omega$, $C_1 = 100\text{nF}$, $C_2 = 100\text{nF}$.



Measured values										Calculated values based on measurements			
The condition $U_2 = 0$					The condition $U_1 = 0$					$ Y_{11} $	$ Y_{12} $	$ Y_{21} $	$ Y_{22} $
$ U_1 $	$ U_{C1} $	$ I_1 $	$ U_{C2} $	$ I_2 $	$ U_2 $	$ U_{C1} $	$ I_1 $	$ U_{C2} $	$ I_2 $				
[V]	[V]	[mA]	[V]	[mA]	[V]	[V]	[mA]	[V]	[mA]	[mS]	[mS]	[mS]	[mS]

4. Determine the parameter values for the two-port network shown in the figure. Work is done with alternating current at a frequency of 10 kHz, and the voltage applied from the generator is 5 Vrms. The following resistors and capacitors are used for the circuit implementation: $R = 600\Omega$, $C_1 = 100\text{nF}$, $C_2 = 100\text{nF}$.

