

First & Last name student 1  
.....  
Dates/Time range .....

First & Last name student 2  
.....  
Lab workstation number .....

### The matrix parameters of the two-port networks

A)  $Z_1 =$   $Z_2 =$

B) Experimental determination of A-parameters  $R_{a1} =$   $R_{a2} =$

Measured values									Calculated values based on measurements											
Condition $I_2 = 0$				Condition $U_2 = 0$					$A_{11}$	$A_{12}$	$A_{21}$	$A_{22}$	$\Delta A$							
$U_1$	$U_2$	$U_{a1}$	$I_1$	$U_1$	$U_{a1}$	$I_1$	$U_{a2}$	$I_2$	[V]	[V]	[mA]	[V]	[mA]	/V]	[mA]	-	[kΩ]	[mS]	-	-

$$\delta = |1 - \Delta A| = \leq 5\%$$

C) Experimental determination of Z-parameters

Measured values								Calculated values based on measurements											
Condition $I_2 = 0$				Condition $I_1 = 0$				$Z_{11}$	$Z_{12}$	$Z_{21}$	$Z_{22}$								
$U_1$	$U_2$	$U_{a1}$	$I_1$	$U_1$	$U_2$	$U_{a2}$	$I_2$	[V]	[V]	/V]	[mA]	[kΩ]	[kΩ]	[kΩ]	[kΩ]	[kΩ]	[kΩ]		

$$\delta = \frac{|Z_{12} - Z_{21}|}{Z_{12}} = \leq 5\%$$

D) The Z-parameters are determined by calculation starting from the A-parameters

$$Z'_{11} = \quad \delta_{11} = \quad Z'_{12} = \quad \delta_{12} =$$

$$Z'_{21} = \quad \delta_{21} = \quad Z'_{22} = \quad \delta_{22} =$$

E) Theoretical and experimental determination of Y-parameters

$$Y_{11t} = \quad |Y_{11t}| = \quad \arg\{Y_{11t}\} =$$

$$Y_{12t} = \quad |Y_{12t}| = \quad \arg\{Y_{12t}\} =$$

$$Y_{21t} = \quad |Y_{21t}| = \quad \arg\{Y_{21t}\} =$$

$$Y_{22t} = \quad |Y_{22t}| = \quad \arg\{Y_{22t}\} =$$

Measured values										Calculated values based on measurements			
Condition $U_2 = 0$					Condition $U_1 = 0$					$ Y_{11} $	$ Y_{12} $	$ Y_{21} $	$ Y_{22} $
$ U_1 $	$ U_{C1} $	$ I_1 $	$ U_{C2} $	$ I_2 $	$ U_2 $	$ U_{C1} $	$ I_1 $	$ U_{C2} $	$ I_2 $				
[V]	[V]	[mA]	[V]	[mA]	[V]	[V]	[mA]	[V]	[mA]	[mS]	[mS]	[mS]	[mS]

Measured values				Calculated values based on measurements			
Condition $U_2 = 0$		Condition $U_1 = 0$		$\arg\{Y_{11}\}$	$\arg\{Y_{21}\}$	$\arg\{Y_{22}\}$	$\arg\{Y_{12}\}$
$\Delta t_{U_{C1}-U_1}$	$\Delta t_{U_{C2}-U_1}$	$\Delta t_{U_{C2}-U_2}$	$\Delta t_{U_{C1}-U_2}$				
[μs]	[μs]	[μs]	[μs]	[°]	[°]	[°]	[°]

Calculation of the error for the magnitudes of the Y-parameters:

$$\delta_{11} =$$

$$\delta_{12} =$$

$$\delta_{21} =$$

$$\delta_{22} =$$

Calculation of the error for the phases of the Y-parameters:

$$\delta_{11} =$$

$$\delta_{12} =$$

$$\delta_{21} =$$

$$\delta_{22} =$$


F)  $H_{U21gt} = |H_{U21gt}| =$

$$U_1 =$$

f [kHz]	0,5	1	1,5	2	2,5	3	3,5	4	4,5	5
$U_2 [V]$										
$ H_{U21g}  = \frac{U_2}{U_1}$										
$ H_{U21g} _t$										

Graph  $|H_{U21g}|$


What type of filter is obtained?.....

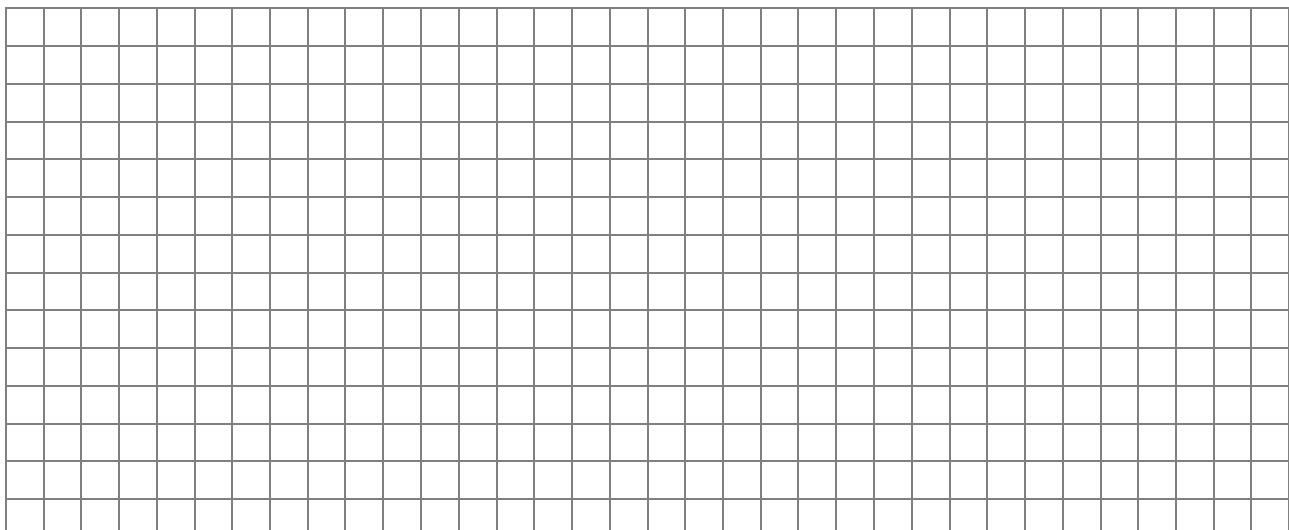

G)  $H_{U21gt} = \arg\{H_{U21gt}\} =$

f [kHz]	0,5	1	1,5	2	2,5	3	3,5	4	4,5	5
$\Delta t$										
$\varphi$ [degrees]										
$\varphi_t$ [degrees]										

Graph  $\arg\{H_{U21g}\}$

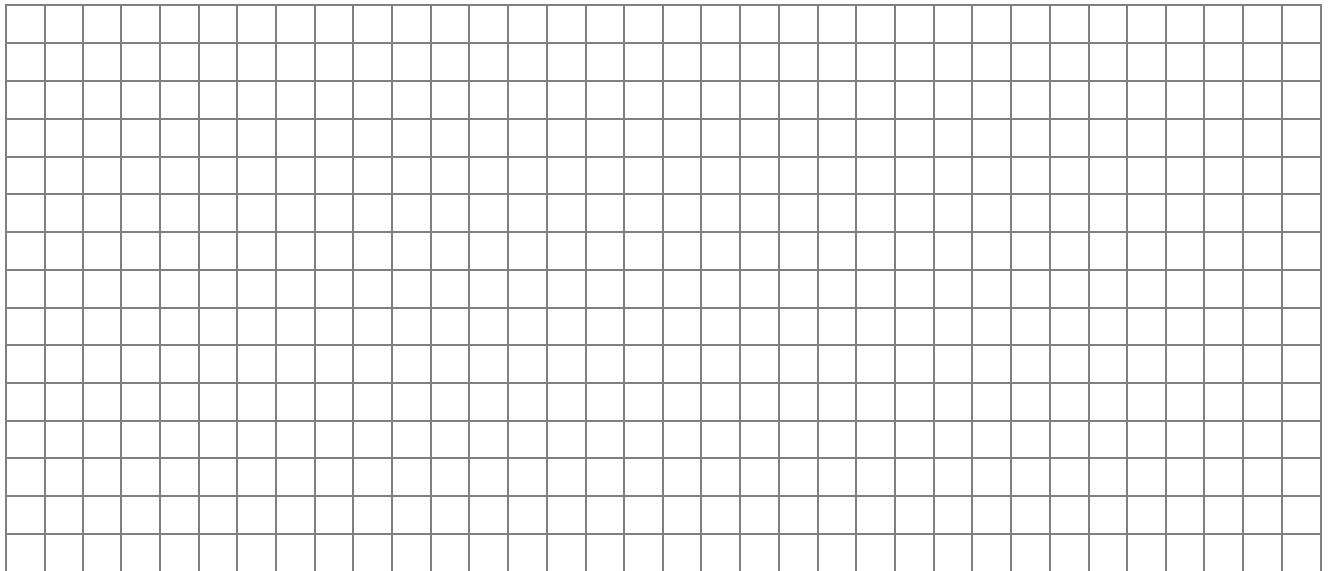

H) Complete the formula and the obtained value:

$$Y_{11t} = |Y_{11t}| = \arg\{Y_{11t}\} =$$

$$Y_{12t} = |Y_{12t}| = \arg\{Y_{12t}\} =$$

$$Y_{21t} = |Y_{21t}| = \arg\{Y_{21t}\} =$$

$$Y_{22t} = |Y_{22t}| = \arg\{Y_{22t}\} =$$

Measured values										Calculated values based on measurements					
Condition $U_2 = 0$					Condition $U_1 = 0$					$ Y_{11} $	$ Y_{12} $	$ Y_{21} $	$ Y_{22} $		
$ U_1 $	$ U_{R1} $	$ I_1 $	$ U_{R2} $	$ I_2 $	$ U_2 $	$ U_{R1} $	$ I_1 $	$ U_{R2} $	$ I_2 $	[V]	[V]	[mA]	[mA]	[mA]	[mA]

Measured values				Calculated values based on measurements			
Condition $U_2 = 0$		Condition $U_1 = 0$		$\arg\{Y_{11}\}$	$\arg\{Y_{21}\}$	$\arg\{Y_{22}\}$	$\arg\{Y_{12}\}$
$\Delta t_{U_{R1}-U_1}$	$\Delta t_{U_{R2}-U_1}$	$\Delta t_{U_{R2}-U_2}$	$\Delta t_{U_{R1}-U_2}$				
[μs]	[μs]	[μs]	[μs]	[°]	[°]	[°]	[°]

Calculation of the error for the Y-parameters module      Calculation of the error for the Y-parameters phase

$$\delta_{11} =$$

$$\delta_{11} =$$

$$\delta_{12} =$$

$$\delta_{12} =$$

$$\delta_{21} =$$

$$\delta_{21} =$$

$$\delta_{22} =$$

$$\delta_{22} =$$


I)       $H_{U21gt} =$        $|H_{U21gt}| =$

$$U_1 =$$

f [kHz]	0,5	1	1,5	2	2,5	3	3,5	4	4,5	5
$U_2 [V]$										
$ H_{U21g}  = \frac{U_2}{U_1}$										
$ H_{U21g} _t$										

Graph  $|H_{U21g}|$

What type of filter is obtained?.....

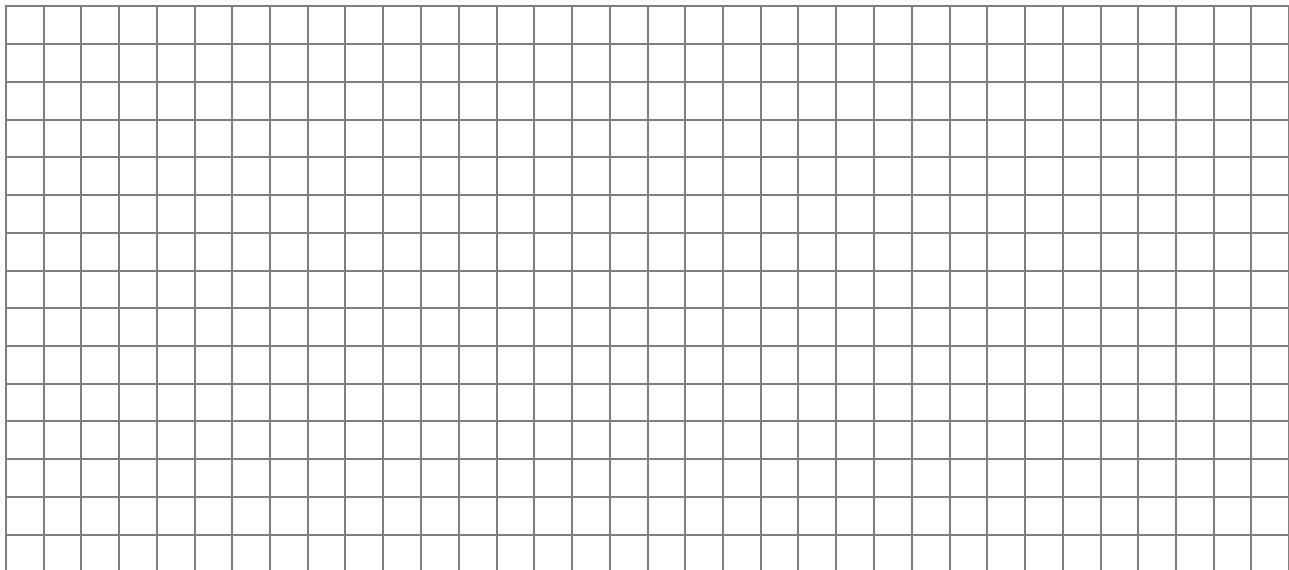

J)       $H_{U21gt} =$        $\arg\{H_{U21gt}\} =$

f [kHz]	0,5	1	1,5	2	2,5	3	3,5	4	4,5	5
$\Delta t$										
$\varphi$ [degrees]										
$\varphi_t$ [degrees]										

Graph  $\arg\{H_{U21g}\}$

